

Q1: RTL is primarily concerned with defining the flow of signals between

- A. Registers
- B. Clock
- C. Inverters
- D. None of the above

Q2: RTL Design only contains combinational circuits and does not include any sequential components

- A. True
- B. False

Q3: RTL is primarily concerned with defining the flow of signals between

- A. Registers
- B. Clock
- C. Inverters
- D. None of the above

Q4: RTL is primarily concerned with defining the flow of signals between

- A. Registers
- B. Clock
- C. Inverters
- D. None of the above